

## Network Theory - Equivalent Circuits

If a circuit consists of two or more similar passive elements and are connected in exclusively of series type or parallel type, then we can replace them with a single equivalent passive element. Hence, this circuit is called as an **equivalent circuit**.


In this chapter, let us discuss about the following two equivalent circuits.

- Series Equivalent Circuit
- Parallel Equivalent Circuit
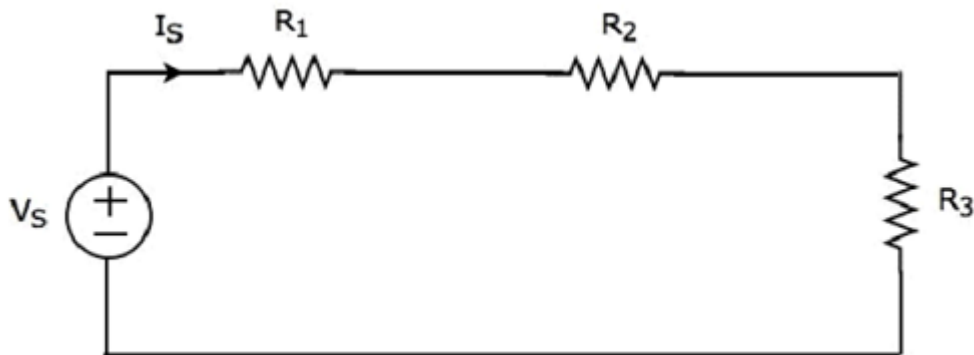
### Series Equivalent Circuit

If similar passive elements are connected in **series**, then the same current will flow through all these elements. But, the voltage gets divided across each element.

Consider the following **circuit diagram**.



It has a single voltage source ( $V_S$ ) and three resistors having resistances of  $R_1$ ,  $R_2$  and  $R_3$ . All these elements are connected in series. The current  $I_S$  flows through all these elements.

The above circuit has only one mesh. The **KVL equation** around this mesh is

$$V_S = V_1 + V_2 + V_3$$

Substitute  $V_1 = I_S R_1$ ,  $V_2 = I_S R_2$  and  $V_3 = I_S R_3$  in the above equation.


$$V_S = I_S R_1 + I_S R_2 + I_S R_3$$

$$\Rightarrow V_S = I_S(R_1 + R_2 + R_3)$$

The above equation is in the form of  $V_S = I_S R_{Eq}$  where,

$$R_{Eq} = R_1 + R_2 + R_3$$

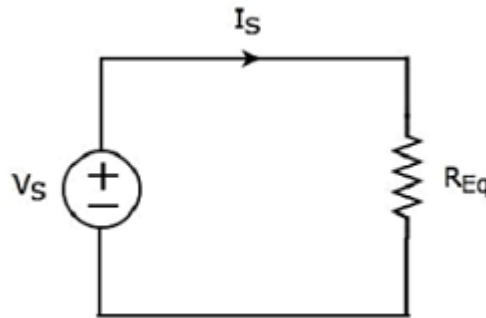The **equivalent circuit diagram** of the given circuit is shown in the following figure.



That means, if multiple resistors are connected in series, then we can replace them with an **equivalent resistor**. The resistance of this equivalent resistor is equal to sum of the resistances of all those multiple resistors.

**Note 1** – If ‘N’ inductors having inductances of  $L_1, L_2, \dots, L_N$  are connected in series, then the **equivalent inductance** will be

$$L_{Eq} = L_1 + L_2 + \dots + L_N$$


**Note 2** – If ‘N’ capacitors having capacitances of  $C_1, C_2, \dots, C_N$  are connected in series, then the **equivalent capacitance** will be

$$\frac{1}{C_{Eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$
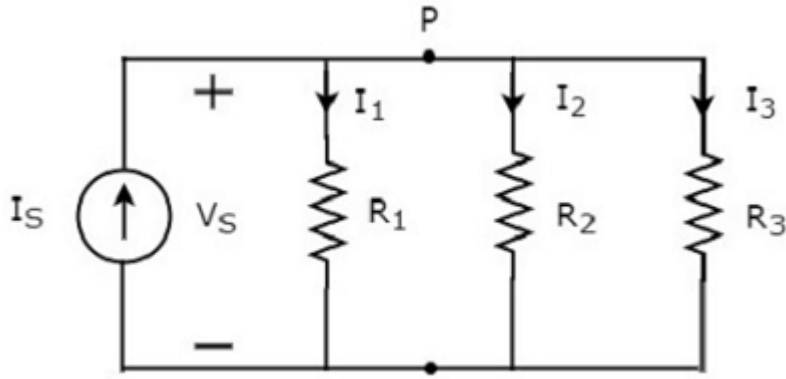
## Parallel Equivalent Circuit

If similar passive elements are connected in **parallel**, then the same voltage will be maintained across each element. But, the current flowing through each element gets divided.

Consider the following **circuit diagram**.



It has a single current source ( $I_S$ ) and three resistors having resistances of  $R_1$ ,  $R_2$ , and  $R_3$ . All these elements are connected in parallel. The voltage ( $V_S$ ) is available across all these elements.

The above circuit has only one principal node (P) except the Ground node. The **KCL equation** at this principal node (P) is

$$I_S = I_1 + I_2 + I_3$$

Substitute  $I_1 = \frac{V_S}{R_1}$ ,  $I_2 = \frac{V_S}{R_2}$  and  $I_3 = \frac{V_S}{R_3}$  in the above equation.

$$I_S = \frac{V_S}{R_1} + \frac{V_S}{R_2} + \frac{V_S}{R_3}$$

$$\Rightarrow I_S = V_S \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\Rightarrow V_S = I_S \left[ \frac{1}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)} \right]$$

The above equation is in the form of  $V_S = I_S R_{Eq}$  where,

$$R_{Eq} = \frac{1}{\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

$$\frac{1}{R_{Eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

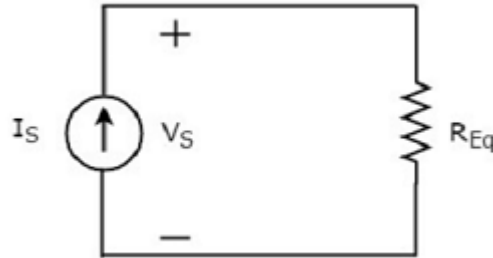The **equivalent circuit diagram** of the given circuit is shown in the following figure.



That means, if multiple resistors are connected in parallel, then we can replace them with an equivalent resistor. The resistance of this **equivalent resistor** is equal to the reciprocal of sum of reciprocal of each resistance of all those multiple resistors.

**Note 1** – If ‘N’ inductors having inductances of  $L_1, L_2, \dots, L_N$  are connected in parallel, then the **equivalent inductance** will be

$$\frac{1}{L_{Eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

**Note 2** – If ‘N’ capacitors having capacitances of  $C_1, C_2, \dots, C_N$  are connected in parallel, then the **equivalent capacitance** will be

$$C_{Eq} = C_1 + C_2 + \dots + C_N$$