

## Network Theory - Mesh Analysis

In Mesh analysis, we will consider the currents flowing through each mesh. Hence, Mesh analysis is also called as **Mesh-current method**.

A **branch** is a path that joins two nodes and it contains a circuit element. If a branch belongs to only one mesh, then the branch current will be equal to mesh current.

If a branch is common to two meshes, then the branch current will be equal to the sum (or difference) of two mesh currents, when they are in same (or opposite) direction.

### Procedure of Mesh Analysis


Follow these steps while solving any electrical network or circuit using Mesh analysis.

- **Step 1** – Identify the **meshes** and label the mesh currents in either clockwise or anti-clockwise direction.
- **Step 2** – Observe the amount of current that flows through each element in terms of mesh currents.
- **Step 3** – Write **mesh equations** to all meshes. Mesh equation is obtained by applying KVL first and then Ohm's law.
- **Step 4** – Solve the mesh equations obtained in Step 3 in order to get the **mesh currents**.


Now, we can find the current flowing through any element and the voltage across any element that is present in the given network by using mesh currents.
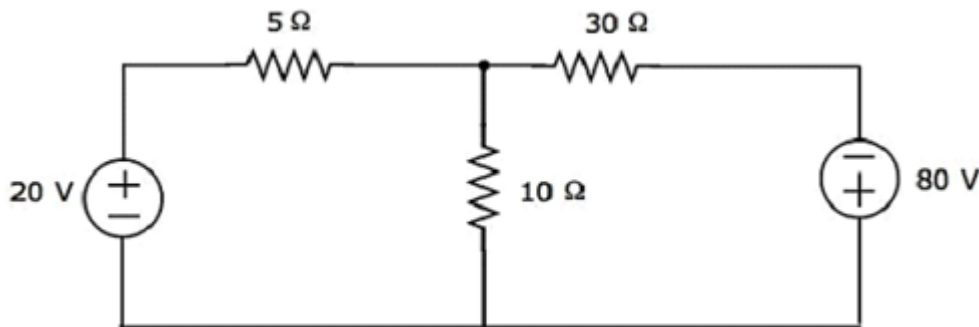
### Example

Find the voltage across  $30\ \Omega$  resistor using **Mesh analysis**.



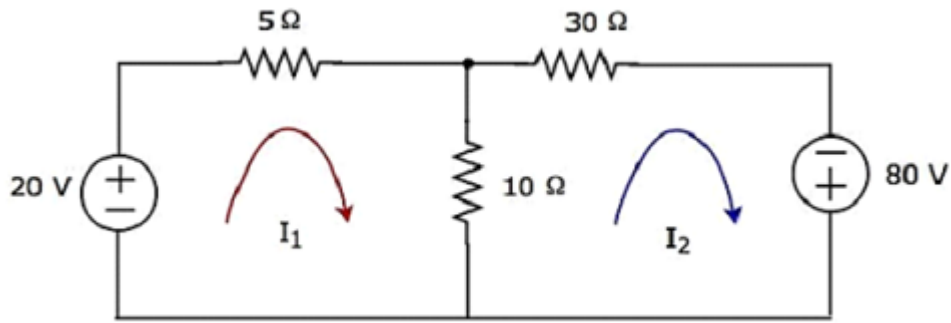**Step 1** – There are two meshes in the above circuit. The **mesh currents**  $I_1$  and  $I_2$  are considered in clockwise direction. These mesh currents are shown in the following figure.



**Step 2** – The mesh current  $I_1$  flows through 20 V voltage source and 5  $\Omega$  resistor. Similarly, the mesh current  $I_2$  flows through 30  $\Omega$  resistor and -80 V voltage source. But, the difference of two mesh currents,  $I_1$  and  $I_2$ , flows through 10  $\Omega$  resistor, since it is the common branch of two meshes.

**Step 3** – In this case, we will get **two mesh equations** since there are two meshes in the given circuit. When we write the mesh equations, assume the mesh current of that particular mesh as greater than all other mesh currents of the circuit.

The **mesh equation** of first mesh is

$$20 - 5I_1 - 10(I_1 - I_2) = 0$$

$$\Rightarrow 20 - 15I_1 + 10I_2 = 0$$

$$\Rightarrow 10I_2 = 15I_1 - 20$$

Divide the above equation with 5.

$$2I_2 = 3I_1 - 4$$

Multiply the above equation with 2.

$$4I_2 = 6I_1 - 8 \quad \text{Equation 1}$$

The **mesh equation** of second mesh is

$$-10(I_2 - I_1) - 30I_2 + 80 = 0$$

Divide the above equation with 10.

$$-(I_2 - I_1) - 3I_2 + 8 = 0$$

$$\Rightarrow -4I_2 + I_1 + 8 = 0$$

$$4I_2 = I_1 + 8$$

**Equation 2**

**Step 4** – Finding mesh currents  $I_1$  and  $I_2$  by solving Equation 1 and Equation 2.

The left-hand side terms of Equation 1 and Equation 2 are the same. Hence, equate the right-hand side terms of Equation 1 and Equation 2 in order to find the value of  $I_1$ .

$$6I_1 - 8 = I_1 + 8$$

$$\Rightarrow 5I_1 = 16$$

$$\Rightarrow I_1 = \frac{16}{5} A$$

Substitute  $I_1$  value in Equation 2.

$$4I_2 = \frac{16}{5} + 8$$

$$\Rightarrow 4I_2 = \frac{56}{5}$$

$$\Rightarrow I_2 = \frac{14}{5} A$$

So, we got the mesh currents  $I_1$  and  $I_2$  as  $\frac{16}{5}$  A and  $\frac{14}{5}$  A respectively.

**Step 5** – The current flowing through 30  $\Omega$  resistor is nothing but the mesh current  $I_2$  and it is equal to  $\frac{14}{5}$  A. Now, we can find the voltage across 30  $\Omega$  resistor by using Ohm's law.

$$V_{30\Omega} = I_2 R$$

Substitute the values of  $I_2$  and  $R$  in the above equation.

$$V_{30\Omega} = \left(\frac{14}{5}\right)30$$

$$\Rightarrow V_{30\Omega} = 84V$$

Therefore, the voltage across 30  $\Omega$  resistor of the given circuit is **84 V**.

**Note 1** – From the above example, we can conclude that we have to solve ‘m’ mesh equations, if the electric circuit is having ‘m’ meshes. That’s why we can choose Mesh analysis when the number of meshes is less than the number of principal nodes (except the reference node) of any electrical circuit.

**Note 2** – We can choose either Nodal analysis or Mesh analysis, when the number of meshes is equal to the number of principal nodes (except the reference node) in any electric circuit.