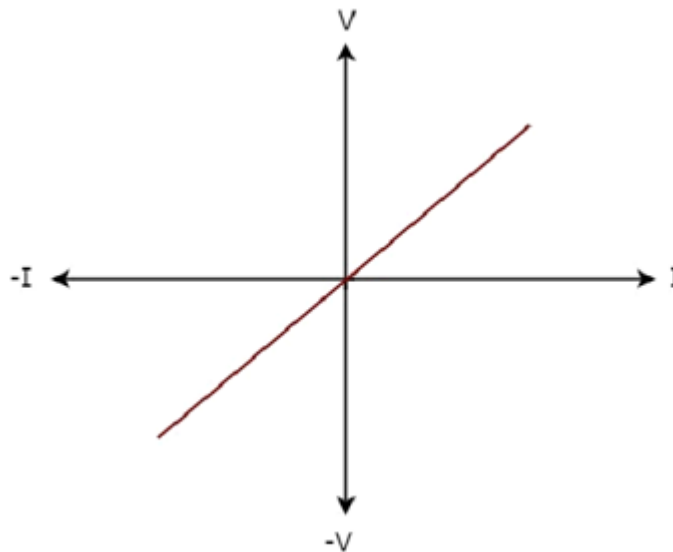


## Network Theory - Example Problems

We discussed the types of network elements in the previous chapter. Now, let us identify the **nature of network elements** from the V-I characteristics given in the following examples.

### Example 1

The **V-I characteristics** of a network element is shown below.



**Step 1** – Verifying the network element as **linear** or **non-linear**.

From the above figure, the V-I characteristics of a network element is a straight line passing through the origin. Hence, it is a **Linear element**.

**Step 2** – Verifying the network element as **active** or **passive**.

The given V-I characteristics of a network element lies in the first and third quadrants.

- In the **first quadrant**, the values of both voltage ( $V$ ) and current ( $I$ ) are positive. So, the ratios of voltage ( $V$ ) and current ( $I$ ) gives positive impedance values.
- Similarly, in the **third quadrant**, the values of both voltage ( $V$ ) and current ( $I$ ) have negative values. So, the ratios of voltage ( $V$ ) and current ( $I$ ) produce positive impedance values.

Since, the given V-I characteristics offer positive impedance values, the network element is a **Passive element**.


**Step 3** – Verifying the network element as **bilateral** or **unilateral**.

For every point  $(I, V)$  on the characteristics, there exists a corresponding point  $(-I, -V)$  on the given characteristics. Hence, the network element is a **Bilateral element**.

Therefore, the given V-I characteristics show that the network element is a **Linear, Passive, and Bilateral element**.
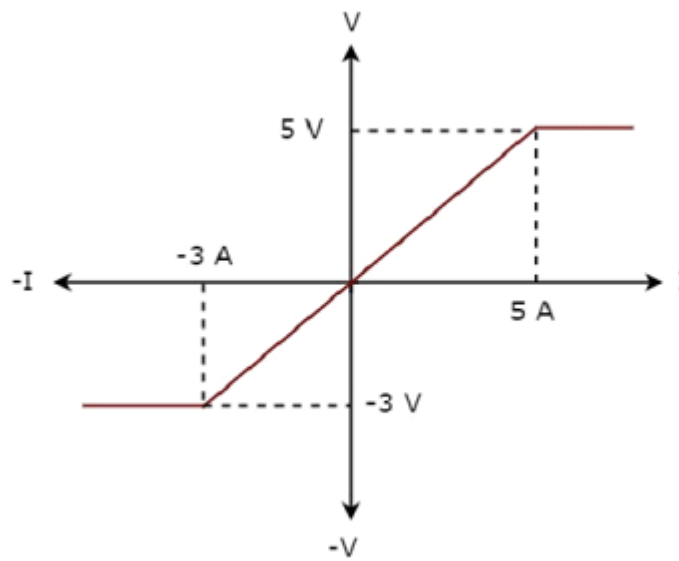
## Example 2

The **V-I characteristics** of a network element is shown below.



**Step 1** – Verifying the network element as **linear** or **non-linear**.

From the above figure, the V-I characteristics of a network element is a straight line only between the points  $(-3\text{ A}, -3\text{ V})$  and  $(5\text{ A}, 5\text{ V})$ . Beyond these points, the V-I characteristics are not following the linear relation. Hence, it is a **Non-linear element**.

**Step 2** – Verifying the network element as **active** or **passive**.

The given V-I characteristics of a network element lies in the first and third quadrants. In these two quadrants, the ratios of voltage ( $V$ ) and current ( $I$ ) produce positive impedance values. Hence, the network element is a **Passive element**.

**Step 3** – Verifying the network element as **bilateral** or **unilateral**.

Consider the point  $(5\text{ A}, 5\text{ V})$  on the characteristics. The corresponding point  $(-5\text{ A}, -3\text{ V})$  exists on the given characteristics instead of  $(-5\text{ A}, -5\text{ V})$ . Hence, the network element is a **Unilateral element**.

Therefore, the given V-I characteristics show that the network element is a **Non-linear, Passive, and Unilateral element**.