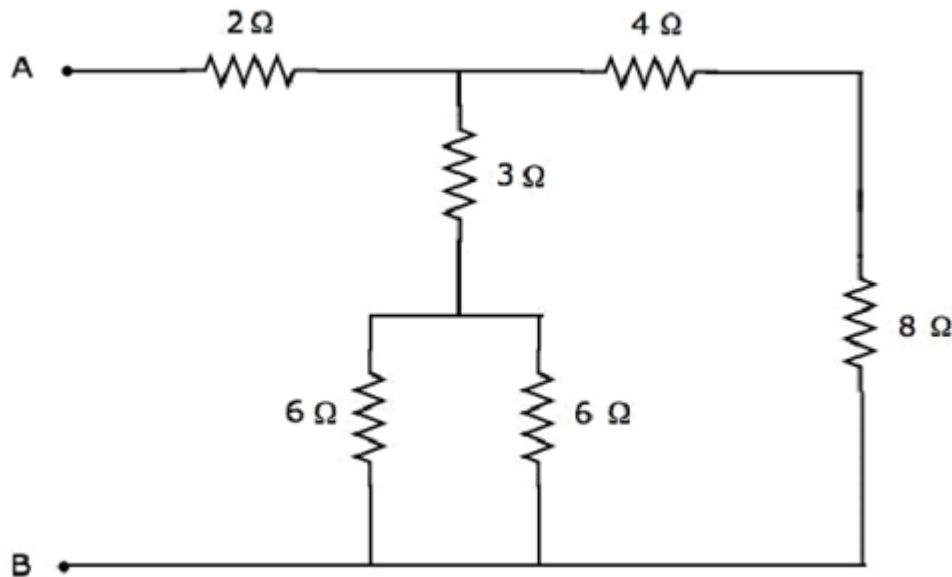


Equivalent Circuits Example Problem

In the previous chapter, we discussed about the equivalent circuits of series combination and parallel combination individually. In this chapter, let us solve an example problem by considering both series and parallel combinations of similar passive elements.


Example

Let us find the **equivalent resistance** across the terminals A & B of the following electrical network.



We will get the equivalent resistance across terminals A & B by minimizing the above network into a single resistor between those two terminals. For this, we have to **identify the combination of resistors** that are connected in series form and parallel form and then find the equivalent resistance of the respective form in every step.

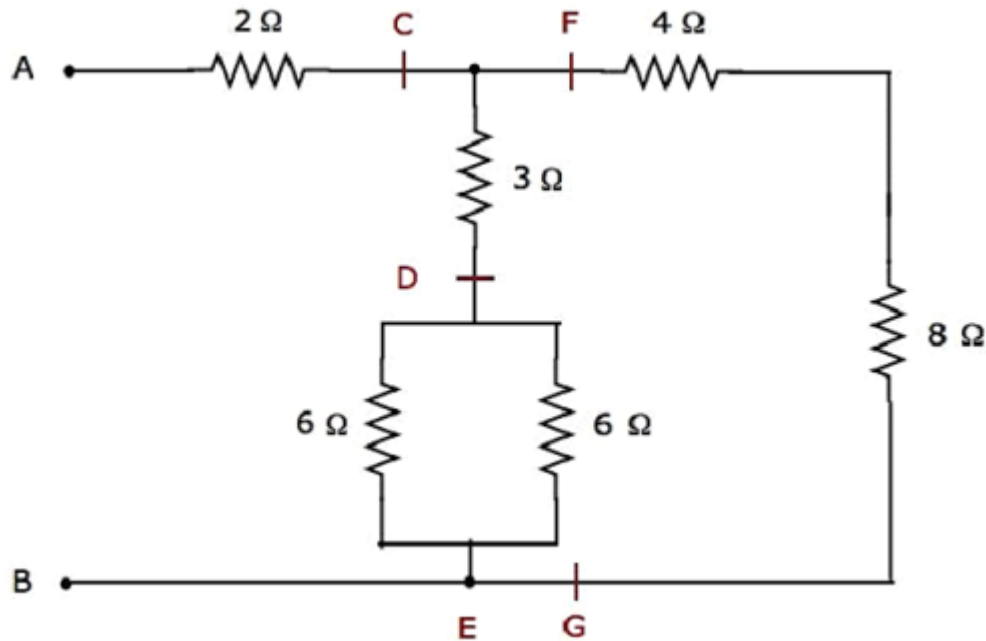The given electrical network is **modified** into the following form as shown in the following figure.



In the above figure, the letters, C to G, are used for labelling various terminals.


Step 1 – In the above network, two **6 Ω resistors** are connected in **parallel**. So, the equivalent resistance between D & E will be 3 Ω. This can be obtained by doing the following simplification.

$$R_{DE} = \frac{6 \times 6}{6 + 6} = \frac{36}{12} = 3\Omega$$

In the above network, the resistors **4 Ω** and **8 Ω** are connected in **series**. So, the equivalent resistance between F & G will be 12 Ω. This can be obtained by doing the following simplification.

$$R_{FG} = 4 + 8 = 12\Omega$$

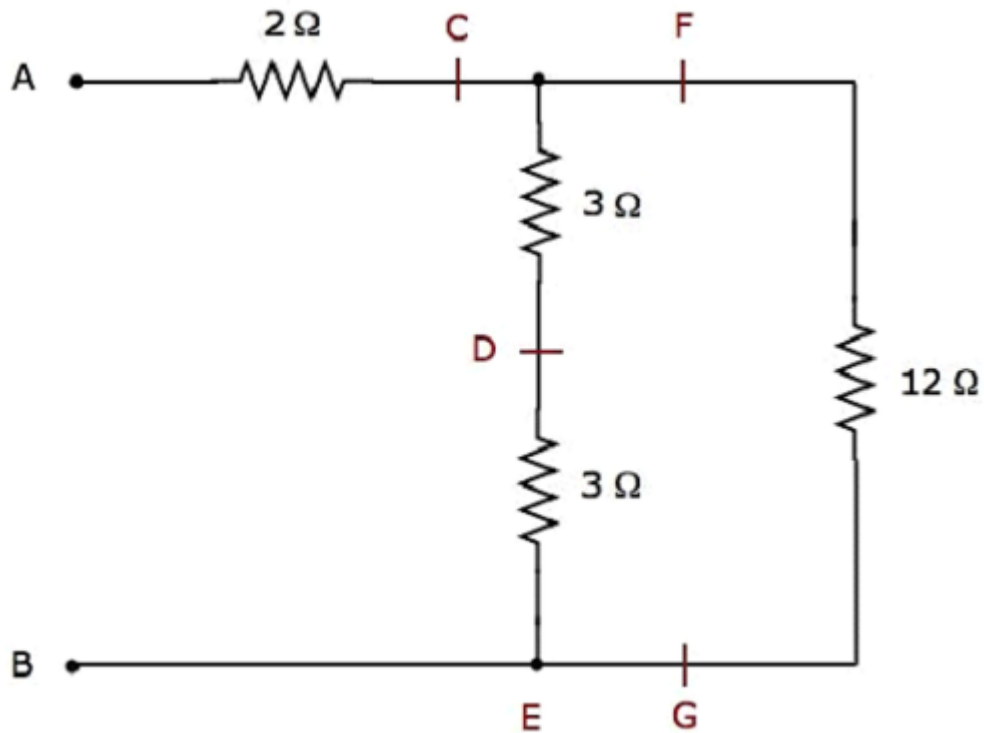
Step 2 – The simplified electrical **network after Step 1** is shown in the following figure.



In the above network, two **3 Ω resistors** are connected in **series**. So, the equivalent resistance between C & E will be **6 Ω**. This can be obtained by doing the following simplification.

$$R_{CE} = 3 + 3 = 6\Omega$$

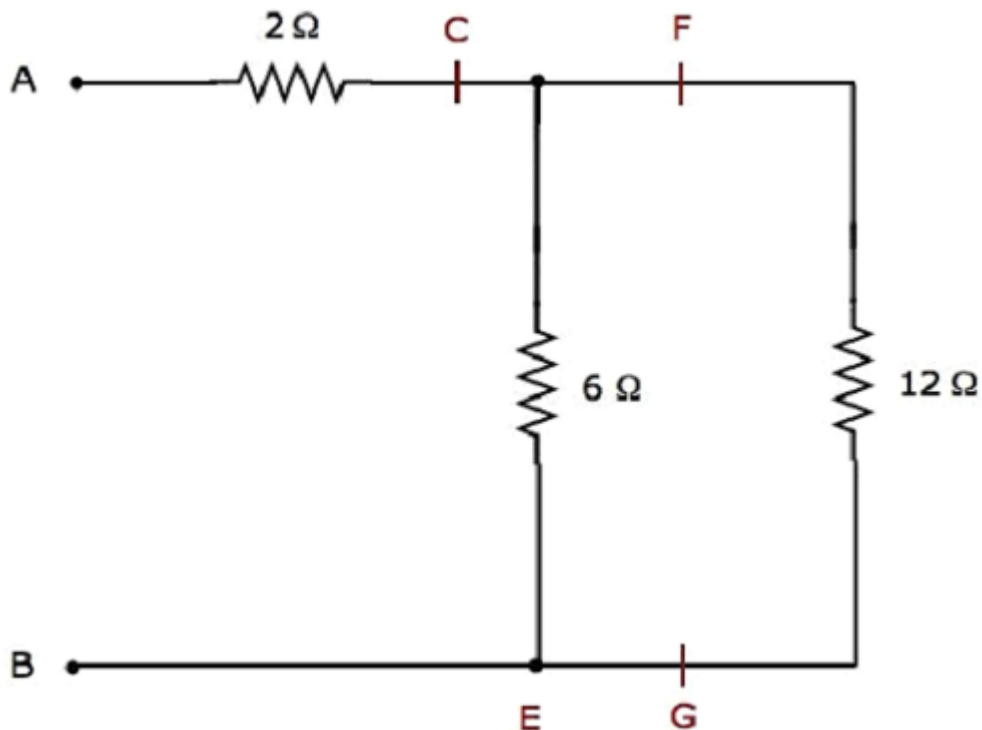
Step 3 – The simplified electrical **network after Step 2** is shown in the following figure.



In the above network, the resistors **6 Ω** and **12 Ω** are connected in **parallel**. So, the equivalent resistance between C & B will be 4 Ω. This can be obtained by doing the following simplification.

$$R_{CB} = \frac{6 \times 12}{6 + 12} = \frac{72}{18} = 4\Omega$$

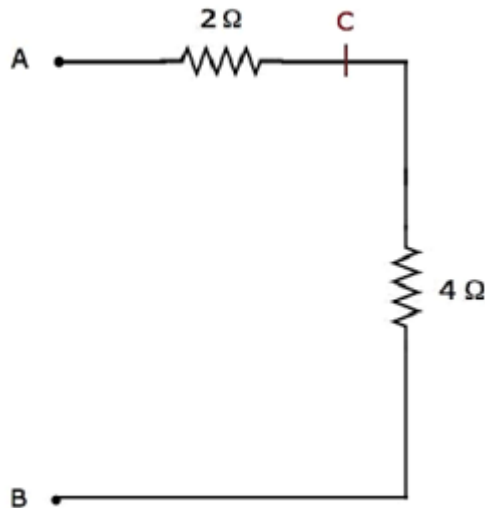Step 4 – The simplified electrical **network after Step 3** is shown in the following figure.



In the above network, the resistors **2 Ω** and **4 Ω** are connected in **series** between the terminals A & B. So, the equivalent resistance between A & B will be 6 Ω. This can be obtained by doing the following simplification.

$$R_{AB} = 2 + 4 = 6\Omega$$

Therefore, the equivalent resistance between terminals A & B of the given electrical network is **6 Ω**.